

ECED2200 - DIGITAL CIRCUITS

Adders, Subtractors, ALUs

GENERAL NOTES

- See updates to these slides: www.newae.com/teaching
- These slides licensed under '[Creative Commons Attribution-ShareAlike 3.0 Unported License](#)'
- These slides are not the complete course – they are extended in-class
- You will find the following references useful, see
www.newae.com/teaching for more information/links:
 - The book “Bebop to the Boolean Boogie” which is available to Dalhousie Students
 - Course notes (covers almost everything we will discuss in class)
 - Various websites such as e.g.: www.play-hookey.com
 - The book “Contemporary Logic Design”, which was used in previous iterations of the class and you may have already

ADDERS & SUBTRACTORS

HALF ADDER

$$\begin{array}{r} 101001 \\ + 010110 \\ \hline \end{array}$$

HALF ADDER

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

HALF ADDER - SUM

A	B	Sum
0	0	0
0	1	1
1	0	1
1	1	0


$$S = m_1 + m_2 = \overline{A} \cdot B + A \cdot \overline{B}$$

HALF ADDER - CARRY

A	B	Carry
0	0	0
0	1	0
1	0	0
1	1	1

$$C = m_3 = A \bullet B$$

HALF ADDER - CIRCUIT

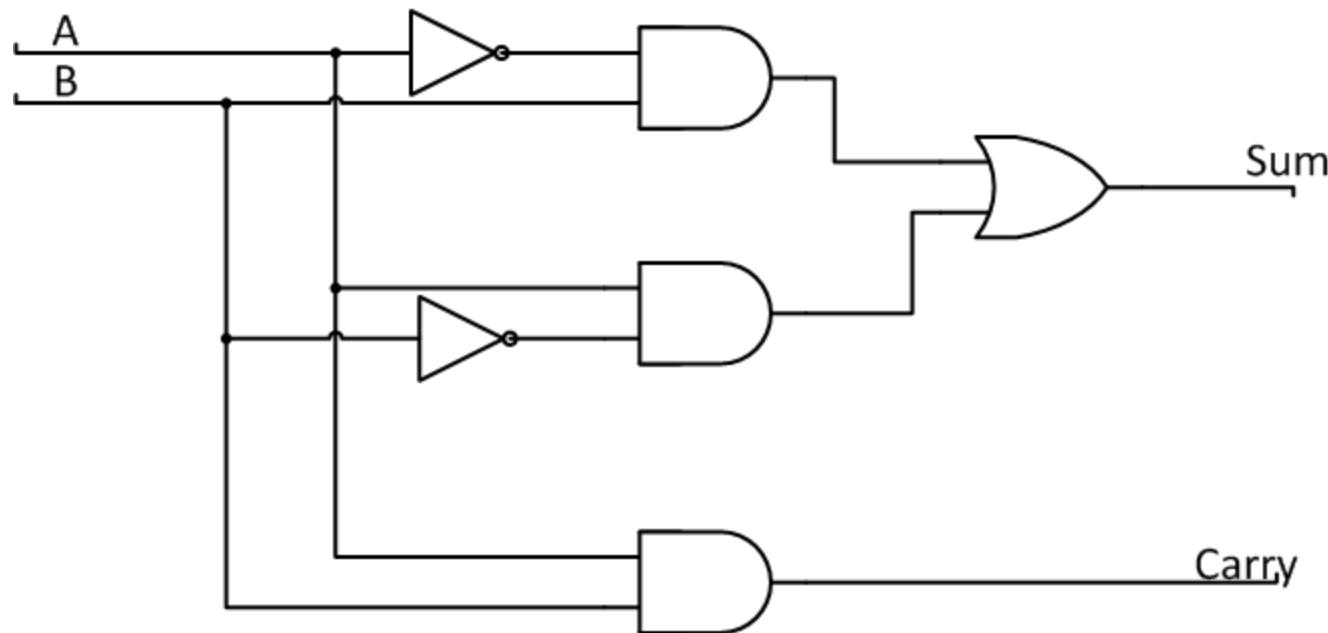

HALF ADDER - CAN WE IMPROVE IT?

$$S = \overline{A} \cdot B + A \cdot \overline{B}$$

No.	Identity	Comments
1	$A+0=A$	Operations with 0 and 1
2	$A+1=1$	Operations with 0 and 1
3	$\underline{A+A=A}$	Idempotent
4	$\underline{A+\overline{A}=1}$	Complements
5	$A \cdot 0=0$	Operations with 0 and 1
6	$A \cdot 1=A$	Operations with 0 and 1
7	$\underline{A \cdot A=A}$	Idempotent
8	$\underline{A \cdot \overline{A}=0}$	Complements
9	$\overline{\overline{A}}=A$	
10	$A+B=B+A$	Commutative
11	$\underline{A \cdot B=B \cdot A}$	Commutative
12	$A+(B+C)=(A+B)+C=A+B+C$	Associative
13	$A \cdot (B \cdot C)=(A \cdot B) \cdot C=A \cdot B \cdot C$	Associative
14	$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$	Distributive
15	$A+(B \cdot C)=(A+B) \cdot (A+C)$	Distributive
16	$A+(A \cdot B)=A$	Absorption
17	$A \cdot (A+B)=A$	Absorption
18	$(A \cdot B)+(\overline{A} \cdot C)+(B \cdot C)=(A \cdot B)+(\overline{A} \cdot C)$	Consensus
19	$\overline{A+B+C+\dots}=\overline{A} \cdot \overline{B} \cdot \overline{C} \dots$	De Morgan
20	$\underline{A \cdot B \cdot C \cdot \dots = A + \overline{B} + \overline{C} \dots}$	De Morgan
21	$(A+\overline{B}) \cdot B=A \cdot B$	Simplification
22	$(A \cdot \overline{B})+B=A+B$	Simplification

HALF ADDER - CAN WE IMPROVE IT?

19)

$$\begin{aligned}
 S &= \overline{\overline{A} \cdot B + A \cdot \overline{B}} \\
 \overline{\overline{C} \bullet \overline{D}} &= \overline{\overline{C} + D} \\
 &= \overline{\overline{A} \cdot B + A \cdot \overline{B}} \\
 &= \overline{A + \overline{B}} + \overline{A + B} \\
 \overline{\overline{C} + \overline{D}} &= \overline{\overline{C} \bullet D} \\
 &= \overline{A + \overline{B} \bullet A + B}
 \end{aligned}$$

20)

No.	Identity	Comments
1	$A+0=A$	Operations with 0 and 1
2	$A+1=1$	Operations with 0 and 1
3	$\underline{A+A=A}$	Idempotent
4	$\underline{A+\overline{A}=1}$	Complements
5	$A \bullet 0=0$	Operations with 0 and 1
6	$A \bullet 1=A$	Operations with 0 and 1
7	$\underline{A \bullet A=A}$	Idempotent
8	$\underline{A \bullet \overline{A}=0}$	Complements
9	$\overline{\overline{A}}=A$	
10	$A+B=B+A$	Commutative
11	$\underline{A \bullet B=B \bullet A}$	Commutative
12	$A+(B+C)=(A+B)+C=A+B+C$	Associative
13	$A \bullet (B \bullet C)=(A \bullet B) \bullet C=A \bullet B \bullet C$	Associative
14	$A \bullet (B+C)=(A \bullet B)+(A \bullet C)$	Distributive
15	$A+(B \bullet C)=(A+B) \bullet (A+C)$	Distributive
16	$A+(A \bullet B)=A$	Absorption
17	$A \bullet (A+B)=A$	Absorption
18	$(A \bullet B) + (\overline{A} \bullet C) + (B \bullet C) = (A \bullet B) + (\overline{A} \bullet C)$	Consensus
19	$\overline{A+B+C+...}=\overline{A} \bullet \overline{B} \bullet \overline{C} ...$	De Morgan
20	$\overline{A \bullet B \bullet C \bullet ...}=\overline{A} + \overline{B} + \overline{C} ...$	De Morgan
21	$(A+\overline{B}) \bullet B=A \bullet B$	Simplification
22	$(A \bullet \overline{B}) + B=A + B$	Simplification

HALF ADDER - CAN WE IMPROVE IT?

$$\begin{aligned}
 &= \overline{\overline{A} + \overline{B} \bullet \overline{A} + B} \\
 &= \overline{(A \bullet \overline{A}) + (A \bullet B) + (\overline{A} \bullet \overline{B}) + (B \bullet \overline{B})} \\
 &= \overline{(0) + (A \bullet B) + (\overline{A} \bullet \overline{B}) + (0)} \\
 &= \overline{(A \bullet B) + (\overline{A} \bullet \overline{B})} \\
 19) \quad &\overline{\overline{C} \bullet \overline{D}} = \overline{C + D} \\
 &= \overline{(\overline{\overline{A}} + \overline{\overline{B}}) + (\overline{A} + B)}
 \end{aligned}$$

No.	Identity	Comments
1	$A+0=A$	Operations with 0 and 1
2	$A+1=1$	Operations with 0 and 1
3	$\underline{A+A=A}$	Idempotent
4	$\underline{A+\overline{A}=1}$	Complements
5	$A \bullet 0=0$	Operations with 0 and 1
6	$A \bullet 1=A$	Operations with 0 and 1
7	$\underline{A \bullet A=A}$	Idempotent
8	$\underline{A \bullet \overline{A}=0}$	Complements
9	$\overline{\overline{A}}=A$	
10	$A+B=B+A$	Commutative
11	$\underline{A \bullet B=B \bullet A}$	Commutative
12	$A+(B+C)=(A+B)+C=A+B+C$	Associative
13	$A \bullet (B \bullet C)=(A \bullet B) \bullet C=A \bullet B \bullet C$	Associative
14	$A \bullet (B+C)=(A \bullet B)+(A \bullet C)$	Distributive
15	$A+(B \bullet C)=(A+B) \bullet (A+C)$	Distributive
16	$A+(A \bullet B)=A$	Absorption
17	$A \bullet (A+B)=A$	Absorption
18	$(A \bullet B) + (\overline{A} \bullet C) + (B \bullet \overline{C}) = (A \bullet B) + (\overline{A} \bullet C)$	Consensus
19	$\overline{A+B+C+...}=\overline{A} \bullet \overline{B} \bullet \overline{C} ...$	De Morgan
20	$\overline{A \bullet B \bullet C \bullet ...}=\overline{A} + \overline{B} + \overline{C} ...$	De Morgan
21	$(A+\overline{B}) \bullet B=A \bullet B$	Simplification
22	$(A \bullet \overline{B}) + B=A + B$	Simplification

HALF ADDER - CAN WE IMPROVE IT?

$$= \overline{\overline{A} + \overline{B}} + \overline{A + B}$$

20) $\overline{\overline{C} + \overline{D}} = \overline{C \bullet D}$

$$= \overline{\overline{A} + \overline{B}} \bullet (A + B)$$


$$= (\overline{A} + \overline{B}) \bullet (A + B)$$

20) $\overline{\overline{C} + \overline{D}} = \overline{C \bullet D}$


$$= (\overline{A \bullet B}) \bullet (A + B)$$

No.	Identity	Comments
1	$A+0=A$	Operations with 0 and 1
2	$A+1=1$	Operations with 0 and 1
3	$A+A=A$	Idempotent
4	$A+\overline{A}=1$	Complements
5	$A \bullet 0=0$	Operations with 0 and 1
6	$A \bullet 1=A$	Operations with 0 and 1
7	$A \bullet A=A$	Idempotent
8	$A \bullet \overline{A}=0$	Complements
9	$\overline{\overline{A}}=A$	
10	$A+B=B+A$	Commutative
11	$A \bullet B=B \bullet A$	Commutative
12	$A+(B+C)=(A+B)+C=A+B+C$	Associative
13	$A \bullet (B \bullet C)=(A \bullet B) \bullet C=A \bullet B \bullet C$	Associative
14	$A \bullet (B+C)=(A \bullet B)+(A \bullet C)$	Distributive
15	$A+(B \bullet C)=(A+B) \bullet (A+C)$	Distributive
16	$A+(A \bullet B)=A$	Absorption
17	$A \bullet (A+B)=A$	Absorption
18	$(A \bullet B) + (\overline{A} \bullet C) + (B \bullet C) = (A \bullet B) + (\overline{A} \bullet C)$	Consensus
19	$\overline{A+B+C+...}=\overline{A} \bullet \overline{B} \bullet \overline{C} ...$	De Morgan
20	$\overline{A \bullet B \bullet C \bullet ...}=\overline{A} + \overline{B} + \overline{C} ...$	De Morgan
21	$(A+\overline{B}) \bullet B=A \bullet B$	Simplification
22	$(A \bullet \overline{B}) + B=A + B$	Simplification

HALF ADDER - IMPROVED IMPLEMENTATION

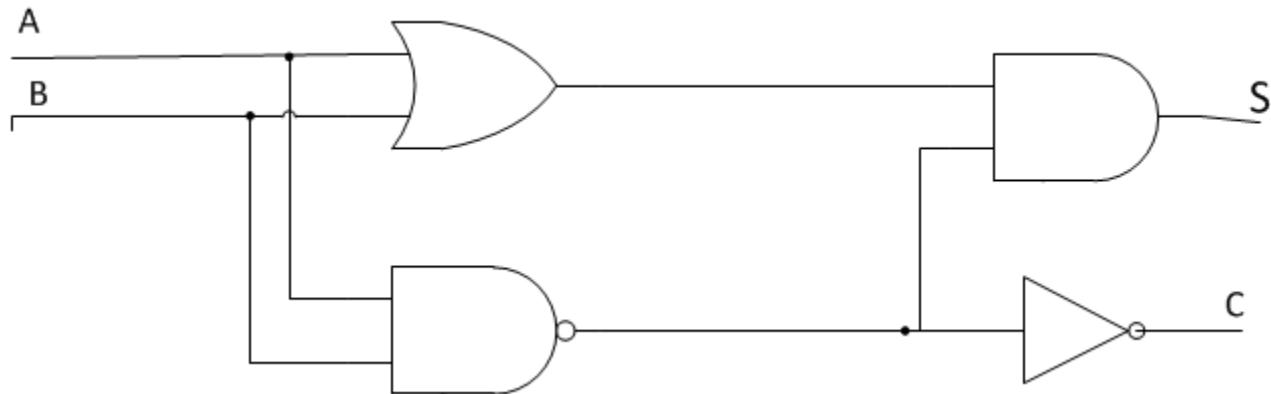

NAND GATE IMPLEMENTATION

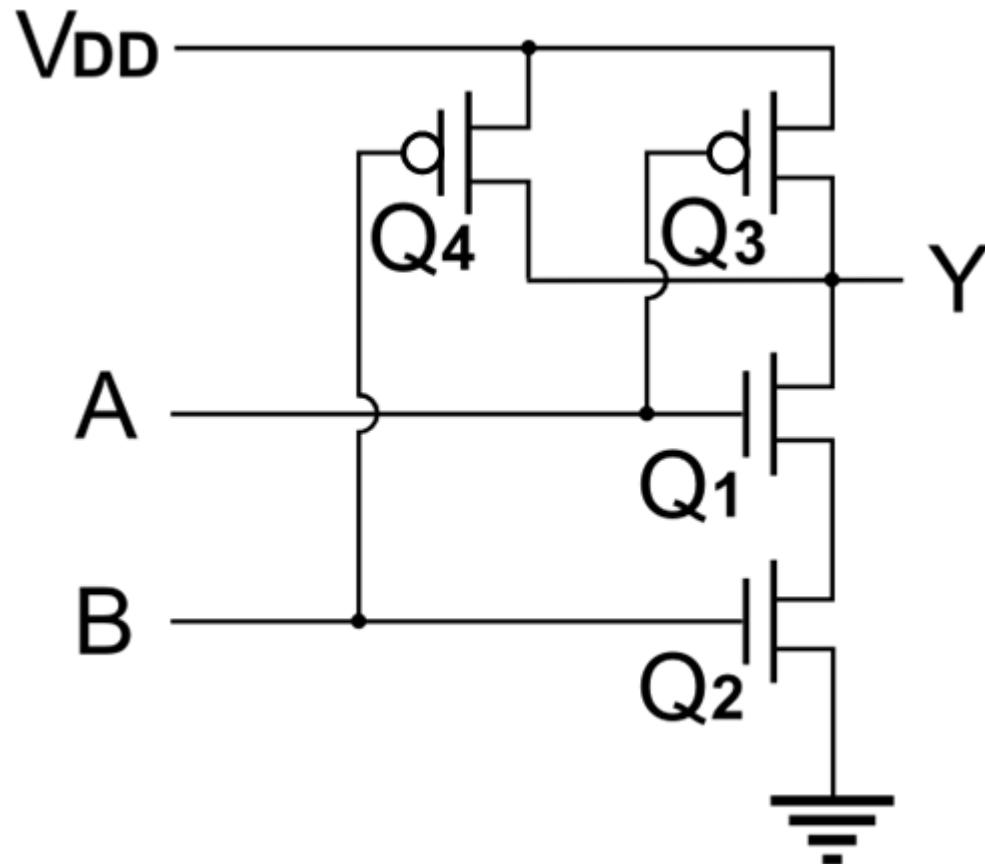


Source: [http://commons.wikimedia.org/wiki/File:NAND_gate_\(CMOS_circuit\).PNG](http://commons.wikimedia.org/wiki/File:NAND_gate_(CMOS_circuit).PNG)

HALF ADDER – EASIER SUM

A	B	Sum
0	0	0
0	1	1
1	0	1
1	1	0

$$S = A \oplus B$$

HALF ADDER - CLASSIC IMPLEMENTATION

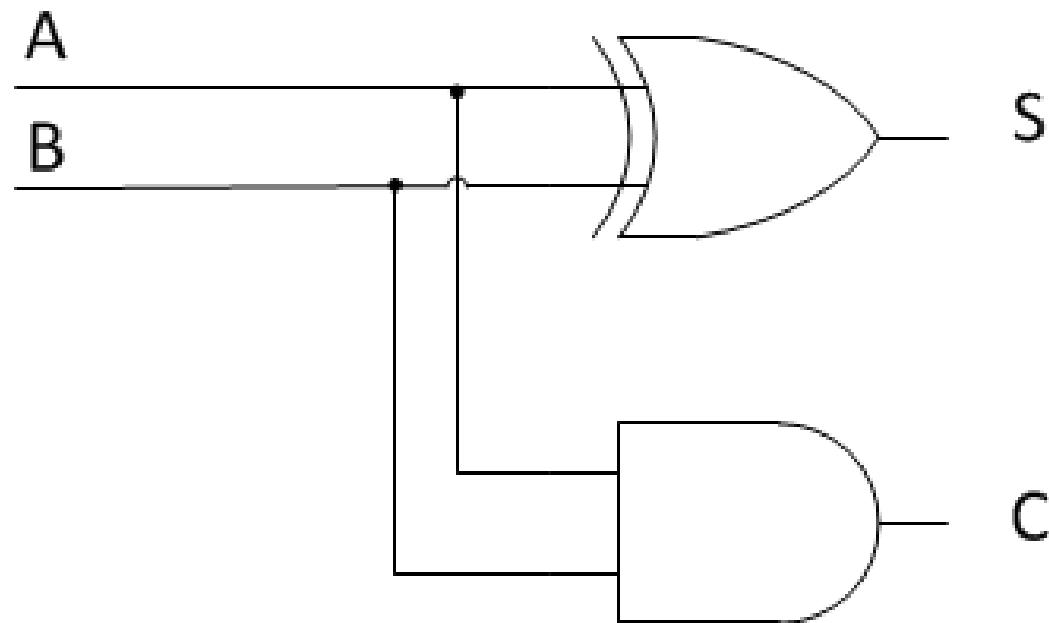

FULL ADDER

$$\begin{array}{r} 101001 \\ + 010110 \\ \hline \end{array}$$

Ci A
B
S
Co

FULL ADDER

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

FULL ADDER - SUM OUT

A	B	Carry In	Sum
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



$$S = m_1 + m_2 + m_4 + m_7$$

FULL ADDER - CARRY OUT


A	B	Carry In	Carry Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$Co = m_3 + m_5 + m_6 + m_7$$

FULL ADDER BUILT FROM HALF ADDERS

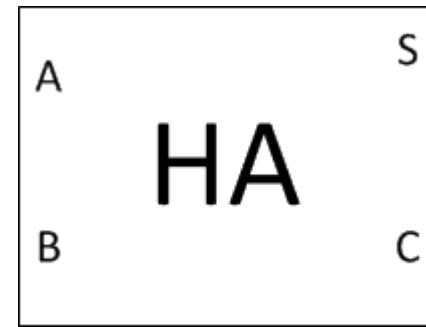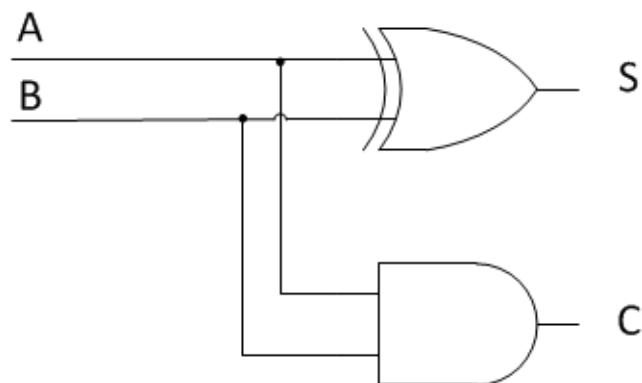


FULL ADDER BUILT FROM HALF ADDERS

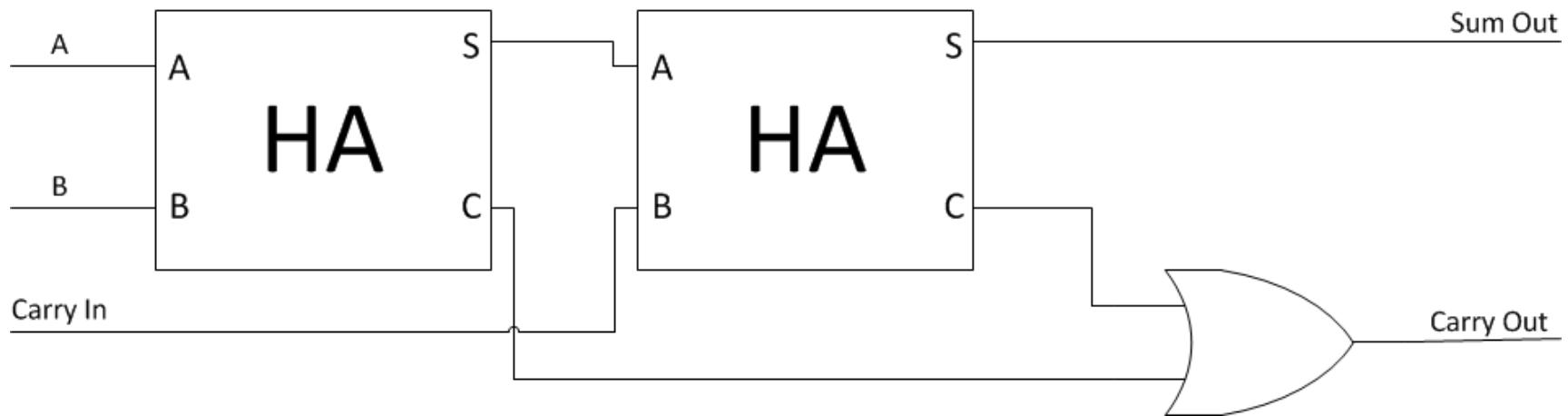


A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

N-BIT ADDERS

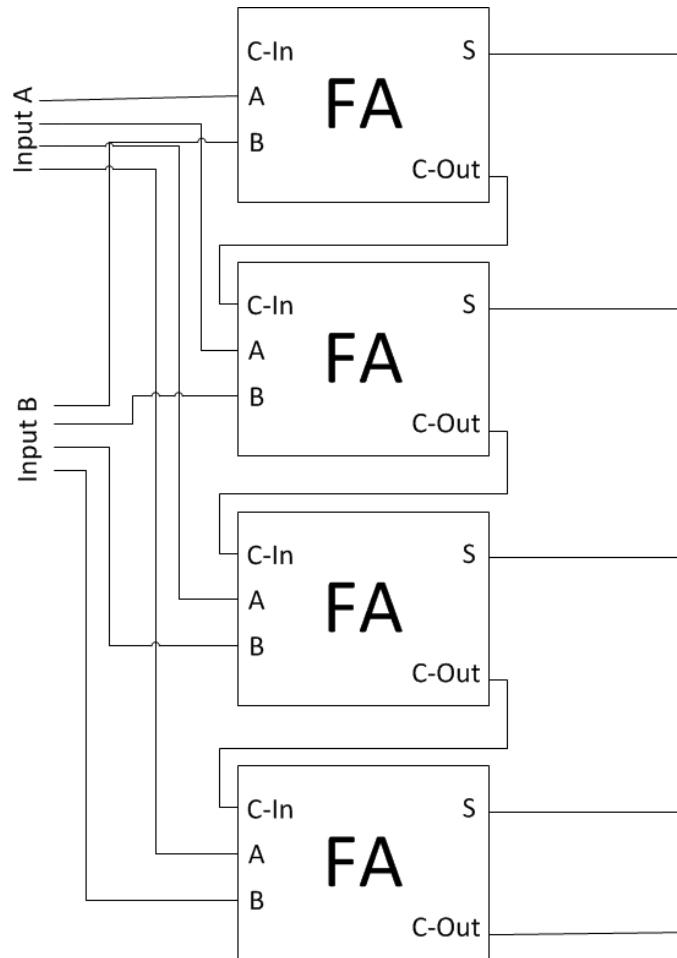

SUBTRACTORS

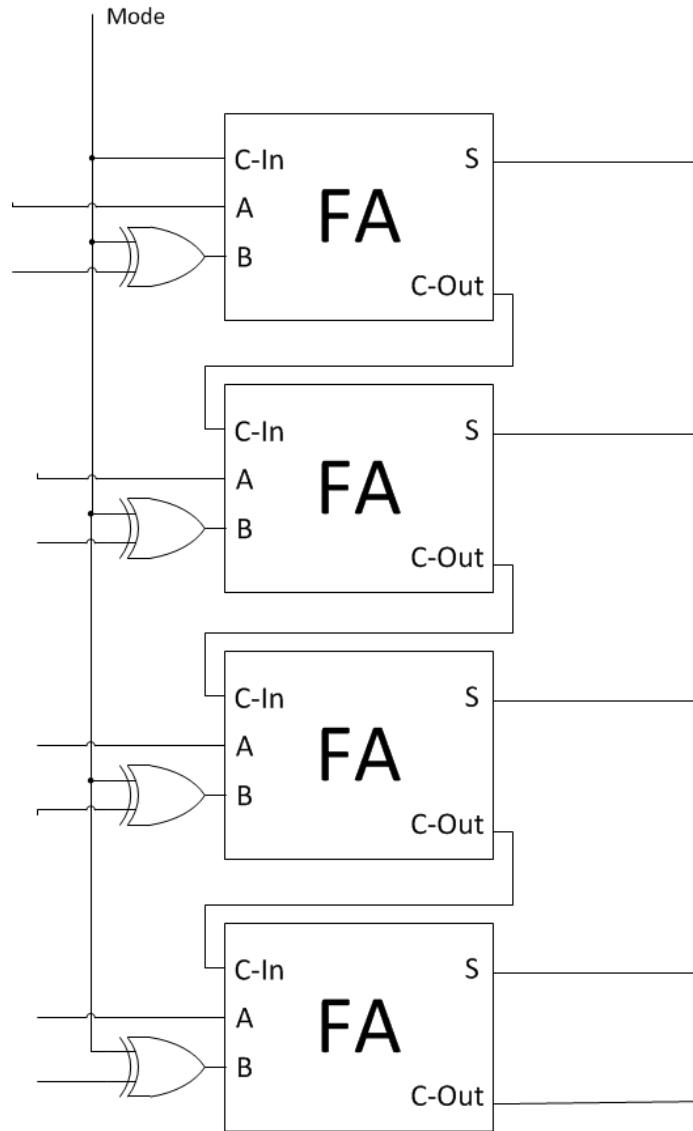

ARITHMETIC LOGIC UNIT (ALU)

ARITHMETIC LOGIC UNIT (ALU)

SECTION SUMMARY

- See ECED Notes “Arithmetic Logic Units” (ALU)
Page 64/65/66