

ECED2200 – DIGITAL CIRCUITS


Introduction, Gates, Number Systems

GENERAL NOTES



- See updates to these slides: www.newae.com/teaching
- These slides licensed under '[Creative Commons Attribution-ShareAlike 3.0 Unported License](https://creativecommons.org/licenses/by-sa/3.0/)'
- These slides are not the complete course – they are extended in-class
- You will find the following references useful, see www.newae.com/teaching for more information/links:
 - The book “Bebop to the Boolean Boogie” which is available to Dalhousie Students
 - Course notes (covers almost everything we will discuss in class)
 - Various websites such as e.g.: www.play-hookey.com
 - The book “Contemporary Logic Design”, which was used in previous iterations of the class and you may have already

INTRODUCTION, BINARY, AND GATES


ANALOG VS. DIGITAL

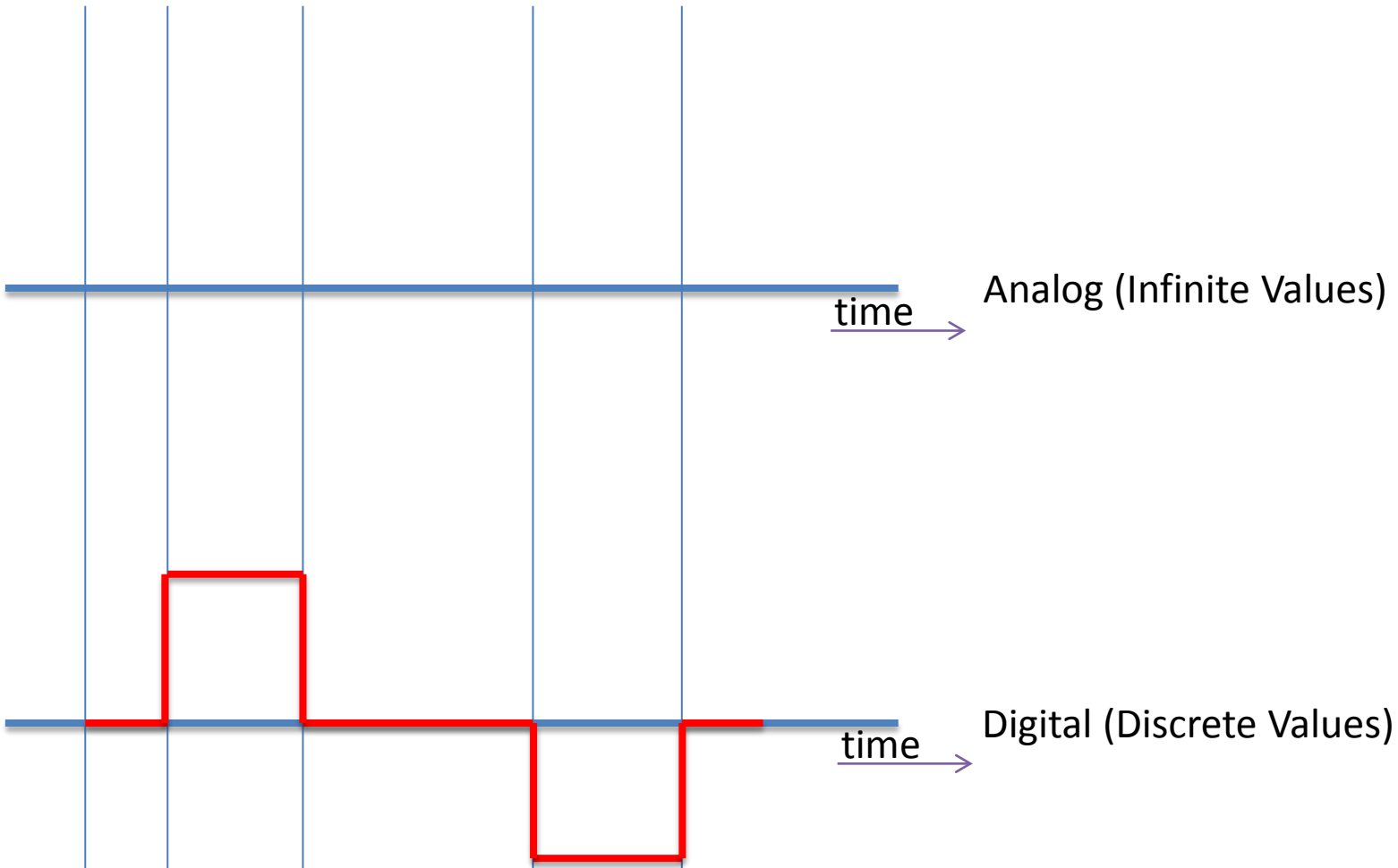


DIGITAL SYSTEMS

  

BINARY

 


Off
False
0
Low

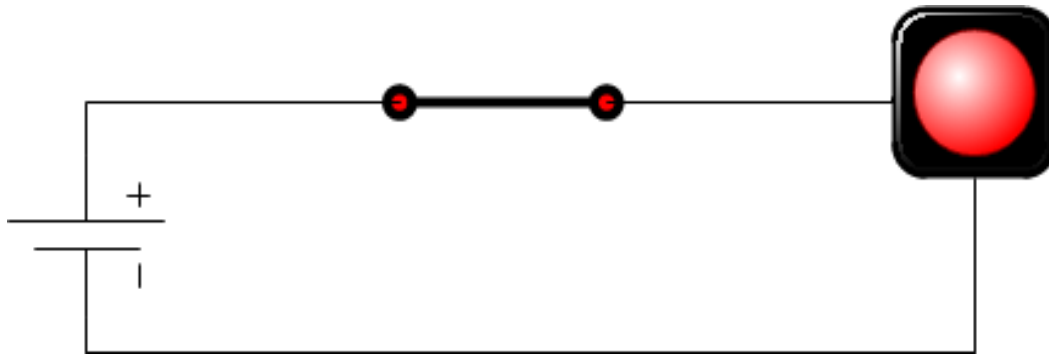


On
True
1
High

BINARY - WAVEFORMS IN TIME

 


GATES

 


OR GATE - TRUTH TABLE

Input #1	Input #2	Output
0	0	0
0	1	1
1	0	1
1	1	1


OR GATE

 


OR GATE

 


OR GATE

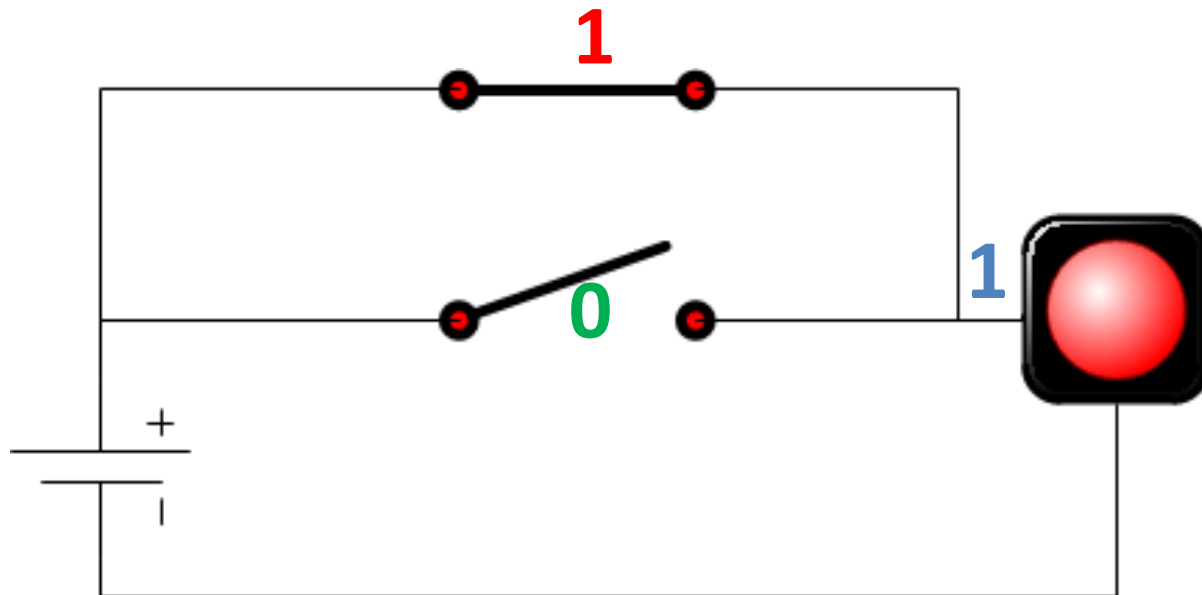

OR GATE

 


OR GATE

 

$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


AND GATE

 

$$Y = A \cdot B$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


NOT GATE

 

$$Y = \overline{A}$$

A	Y
0	1
1	0

EXAMPLE!

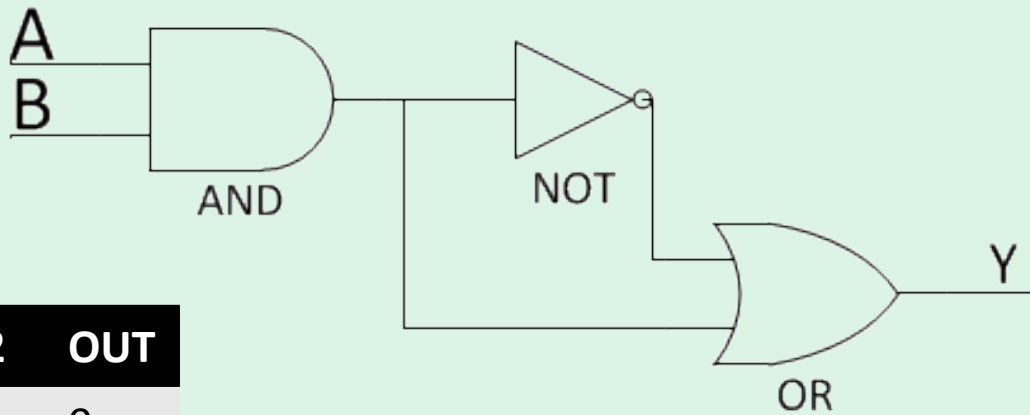

AND

IN1	IN2	OUT
0	0	0
0	1	0
1	0	0
1	1	1

NOT

IN1	OUT
0	1
1	0


OR

IN1	IN2	OUT
0	0	0
0	1	1
1	0	1
1	1	1

Fill in this table:


A	B	Y
0	0	
0	1	
1	0	
1	1	

EXAMPLE!

 




What is the Boolean function of the above schematic?

EXAMPLE!

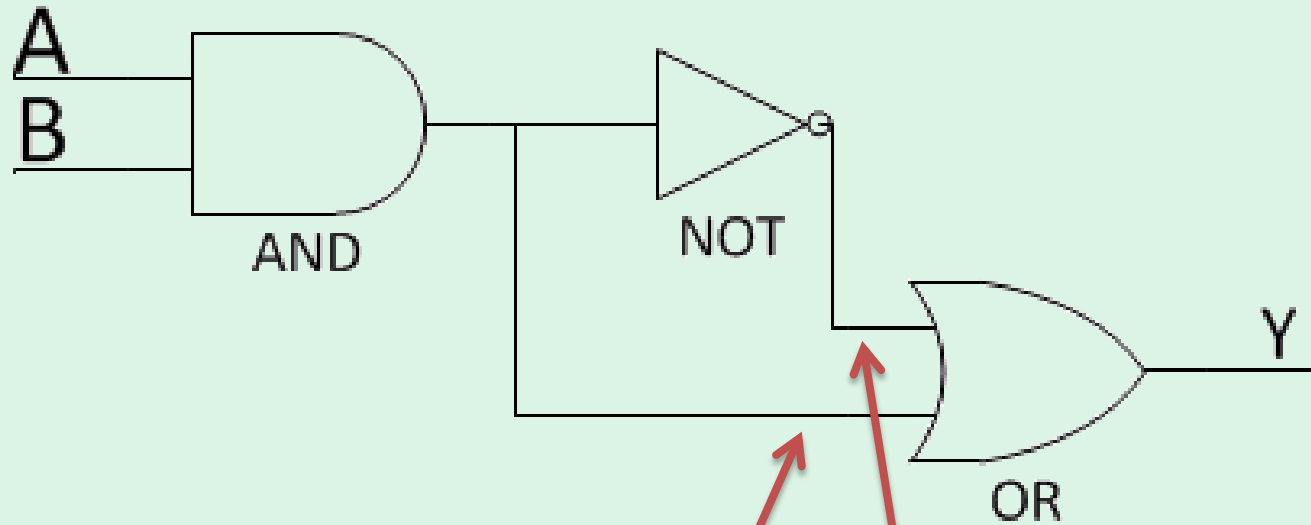


$$Y = A \cdot B + \overline{A} \cdot B$$

LITTLE CIRCLES

   


NOT AND = NAND GATE

 

$$Y = \overline{A \cdot B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOT OR = NOR GATE

 

$$Y = \overline{A+B}$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

SUPERGATES

 


All basic logic operations can be formed with NAND gates (or NOR gates).

EXAMPLE!

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

EXAMPLE!

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

If we inverted each of the A & B inputs to the NAND gate, note we get the same truth table as the OR gate!


EXAMPLE!

 

$$Y = \overline{A} \cdot \overline{B} = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


EXAMPLE!

 


$$Y = \overline{\overline{A} \cdot \overline{B}} = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


WHY DO YOU CARE?

 

EXAMPLE - AND GATE

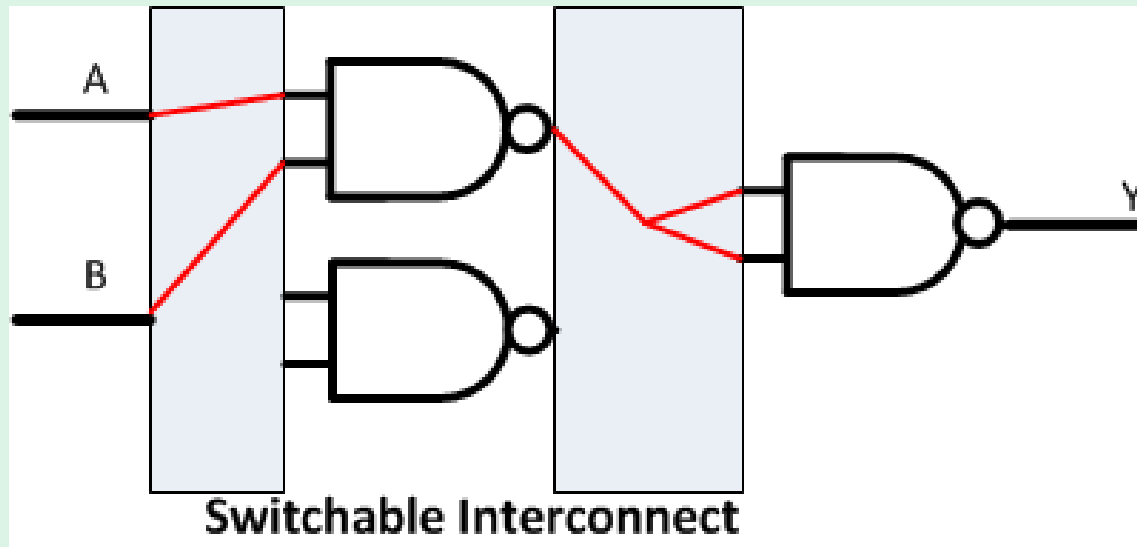


EXCLUSIVE OR (X-OR) GATE

 

$$Y = A \oplus B$$


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR GATE IMPLEMENTATION

 

$$A \oplus B = (A + B) \cdot \overline{(A \cdot B)} = \overline{A} \cdot B + A \cdot \overline{B}$$

EXCLUSIVE NOR (X-NOR) GATE

 

$$Y = A \odot B$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

SECTION SUMMARY - 1/3

Gates have inputs & outputs. Inputs are binary (Boolean) variables with two possible values '1' (True) or '0' (False).

The 'Truth Table' is a table showing every possible input & the resulting output. Different gates have different truth tables.

SECTION SUMMARY - 2/3


The following are the basic gates:



AND




NAND

 

OR




NOR

 


XOR



XNOR

 


Buffer

 

NOT

SECTION SUMMARY - 3/3

 Based on the truth tables, one can make any of the gates with NAND (or NOR) gates. E.g. making an OR gate with NAND gates:



$$Y = \overline{\overline{A} \cdot \overline{B}} = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


REFERENCES / READING

- ECED2200 Notes, “Digital Circuits” section
- Bebop to the Boolean Boogie, Chapter 5
- CLD, Chapter 1


PHYSICAL GATE IMPLEMENTATION

SWITCH LOGIC


OR Gate

 


NOT Gate

 


AND Gate

 


SWITCH NOT

 


SWITCH NOT

 


SWITCH NOT

 


FIELD EFFECT TRANSISTOR SWITCH

 

FET LOGIC GATES - INVERTER (NOT)

 


FET LOGIC GATES - INVERTER (NOT)

 


CMOS = Complementary MOS (e.g.: uses both positive & negative MOS)

FET LOGIC GATES - NAND

 

Source: [http://commons.wikimedia.org/wiki/File:NAND_gate_\(CMOS_circuit\).PNG](http://commons.wikimedia.org/wiki/File:NAND_gate_(CMOS_circuit).PNG)

FET LOGIC GATES - NOR

 

http://commons.wikimedia.org/wiki/File:NOR_gate_%28CMOS_circuit%29.PNG

05/07/2012

Colin O'Flynn - CC BY-SA





LOGIC FAMILIES (TYPES)

1. Diode Logic (DL)
2. Resistor-Transistor Logic (RTL)
3. Diode-Transistor Logic (DTL)
4. Transistor-Transistor Logic (TTL)
5. Metal-Oxide Semiconductor (MOS)
6. **Complementary MOS (CMOS)**
7. Emitter-Coupled Logic (ECL)
8. BiCMOS



CHARACTERISTICS OF LOGIC TYPES

- Fan-in
- Fan-out
- Speed
- Noise Margin
- Power
- Size

SECTION SUMMARY

- Bebop to the Boolean Boogie Chapter 6
- ECED2200 Notes “Electric Switches + Logic Classifications”

NUMBER SYSTEMS



BINARY TO DECIMAL

1110 1011

$2^7=128$ $2^6=64$ $2^5=32$ $2^4=16$ $2^3=8$ $2^2=4$ $2^1=2$ $2^0=1$

1	1	1	0	1	0	1	1
---	---	---	---	---	---	---	---

128 + 64 + 32 + + 8 + + 2 + 1

= 235 Decimal

LET'S DO A HAND-OUT: INTRO-1 (TOP)

Digital Circuits - In Class Handout INTRO-1-V1

Digital Circuits – Binary to Digital Handout

Student Name: _____ Student Number: _____ Date: _____

Convert the Following from Binary to Decimal

$1,0101_2 = \underline{\hspace{2cm}}$

$0,010110_2 = \underline{\hspace{2cm}}$


$111110101001011_2 = \underline{\hspace{2cm}}$

Convert the Following from Decimal to Binary

$12_{10} = \underline{\hspace{2cm}}$

$345_{10} = \underline{\hspace{2cm}}$

$10001 = \underline{\hspace{2cm}}$

 This work by Colin O'Flynn is licensed under a Creative Commons Attribution-ShareAlike, 3.0 Unported License .
CC BY-SA

DECIMAL TO BINARY

216 Decimal

$$216 - 128 = 88 \text{ (1 in } 2^7 \text{ position)}$$

$$88 - 64 = 24 \text{ (1 in } 2^6 \text{ position)}$$

$$24 - 32 < 0, \text{ so 0 in } 2^5 \text{ position}$$

$$24 - 16 = 8 \text{ (1 in } 2^4 \text{ position)}$$

$$8 - 8 = 0 \text{ (1 in } 2^3 \text{ position)}$$

0 in remaining positions

$$2^7=128 \quad 2^6=64 \quad 2^5=32 \quad 2^4=16 \quad 2^3=8 \quad 2^2=4 \quad 2^1=2 \quad 2^0=1$$

1	1	0	1	1	0	0	0
---	---	---	---	---	---	---	---

LET'S DO A HAND-OUT: INTRO-1 (BOTTOM)

Digital Circuits - In Class Handout INTRO-1-V1

Digital Circuits – Binary to Digital Handout

Student Name: _____ Student Number: _____ Date: _____

Convert the Following from Binary to Decimal

1,0 1 0 1₂ = _____

0,0 1 0 1 1 0₂ = _____


1 1 1 1 1 0 1 0 1 0 0 1 0 1 1₂ = _____

Convert the Following from Decimal to Binary

12₁₀ = _____

345₁₀ = _____

10001 = _____

 This work by Colin O'Flynn is licensed under a Creative Commons Attribution-ShareAlike, 3.0 Unported License .
CC BY-SA

NUMBER NOTATION

There are 10 kinds of people in the world – those that understand binary, and those that don't.

NUMBER NOTATION

Ambiguity unacceptable - we are engineers not comics.



$$10_2 = 10_B = 2_{10} \text{ (2 decimal)}$$

$$10_{10} = 10_D = 1010_2 \text{ (1010 binary)}$$

e.g.: Conversion:

$$472_{10} = 111011000$$

HOW TO CHECK YOUR CONVERSIONS

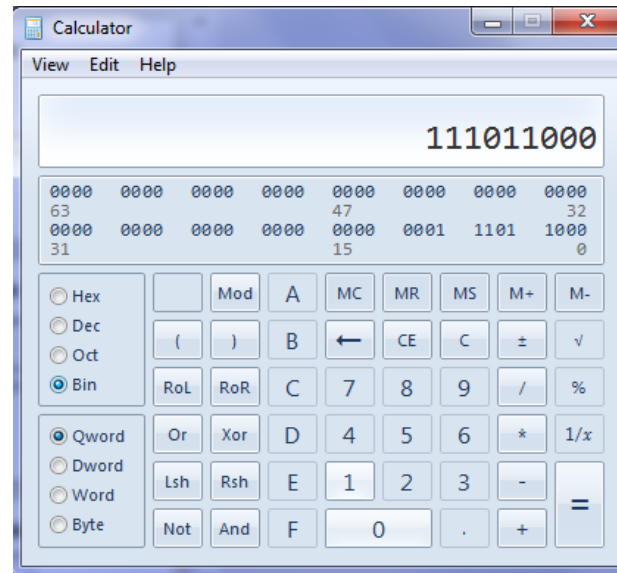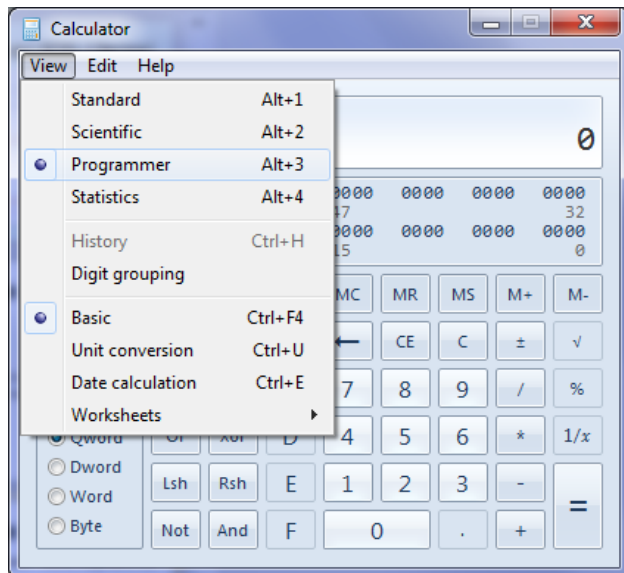

Windows Calculator (Windows 7 version shown)

HOW TO CHECK YOUR CONVERSIONS

Stand Alone Calculator

OTHER NUMBER SYSTEMS: HEX & OCTAL

CHEAT SHEET

Decimal	Binary	Hexadecimal (0x)	Octal (0)
0	0000	0	0
1	0001	1	1
2	0010	2	2
3	0011	3	3
4	0100	4	4
5	0101	5	5
6	0110	6	6
7	0111	7	7
8	1000	8	10
9	1001	9	11
10	1010	A	12
11	1011	B	13
12	1100	C	14
13	1101	D	15
14	1110	E	16
15	1111	F	17

ADVANTAGES OF HEX (AND OCTAL)

1010 1000 1101 1111 1011 0010₂

This is only 24 bits – but long/hard to write...

Equivalent to 11067314₁₀

Easier to write, but conversion is error-prone,
plus we are normally lazy...

ADVANTAGES OF HEX

1010 1000 1101 1111 1011 0010₂



A

8

D

F

B


2

= 0xA8DFB2

Much easier to write, easy to convert!

ADVANTAGES OF OCTAL

101 010 001 101 111 110 110 010₂

 

5 2 1 5 7 6 6 2

= 052157662 in Octal

Easy to write (longer than hex though),
still easy to convert!

BINARY CODED DECIMAL

SECTION SUMMARY

- Bebop to the Boolean Boogie: Chapter 7
- ECED2200 Notes: “Number Systems”


ADDING & SUBTRACTING IN BINARY

ADDING IN BINARY

SUBTRACTING IN BINARY

POSITIVE & NEGATIVE NUMBERS

NUMBER WHEEL

 

DISADVANTAGE OF SIGN MAGNITUDE


- Two Zeros
- Positive & Negative numbers require different processing or else addition is wrong:

$$(-5) + (+1) = 1101 + 0001 = 1110 = -6$$

$$(-3) + (-2) = 1011 + 1010 = 0101 = +5$$

TWO ZEROS? WHERE DID ZERO EVEN COME FROM?

KS

 

Rules of Brahmagupta (628 AD):

- The sum of zero and a negative number is negative.
- The sum of zero and a positive number is positive.
- The sum of zero and zero is zero.
- The sum of a positive and a negative is their difference; or, if their absolute values are equal, zero.

COMPLEMENTARY NUMBERS

DIMINISHED RADIX COMPLEMENT

RADIX COMPLEMENT

2'S COMPLEMENT

1 1 0 1 0 0 0 1 0 0

INSTRUCTIONS

1. Form 1's complement by inverting all bits
2. Add 1 to 1's complement to get 2's complement

2'S COMPLEMENT

1 1 0 1 0 0 0 1 0 0

BIT NOTATIONS

$$2^7=128 \quad 2^6=64 \quad 2^5=32 \quad 2^4=16 \quad 2^3=8 \quad 2^2=4 \quad 2^1=2 \quad 2^0=1$$

--	--	--	--	--	--	--	--

INSTRUCTIONS:

1. Starting from Least Significant Bit (LSB) working towards Most Significant Bit (MSB), copy number one bit at a time.
2. Continue copying until you reach the first '1'. Copy this '1' bit as-is
3. For remaining bits invert them (0->1, 1->0)


SOME EXAMPLES

1 0 1 0 0 1 0 1 0 1 1 0

0 0 1 1 1 1 1 1 0 0 0 1



NUMBER WHEEL

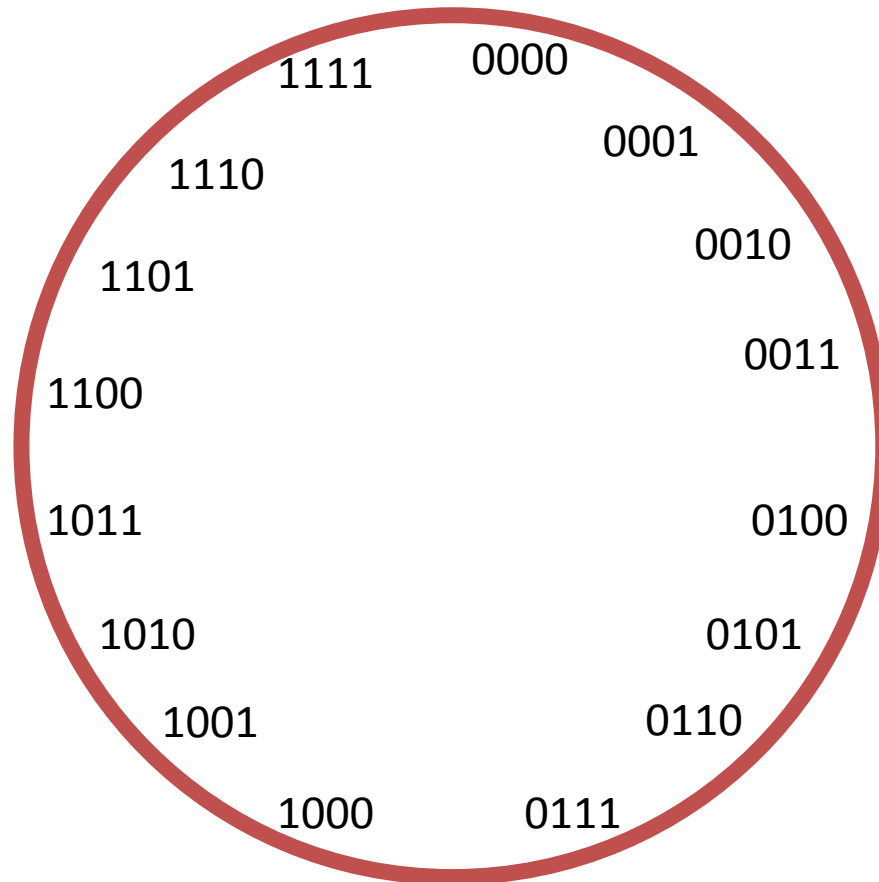

SECTION SUMMARY

- Bebop to the Boolean Boogie: Chapter 8
- Contemporary Logic Design:
- ECED Notes: “Number Systems”