

ECED2200 – DIGITAL CIRCUITS

Multiplexor & Demultiplexor

GENERAL NOTES


- See updates to these slides: www.newae.com/teaching
- These slides licensed under ‘[Creative Commons Attribution-ShareAlike 3.0 Unported License](https://creativecommons.org/licenses/by-sa/3.0/)’
- These slides are not the complete course – they are extended in-class
- You will find the following references useful, see www.newae.com/teaching for more information/links:
 - The book “Bebop to the Boolean Boogie” which is available to Dalhousie Students
 - Course notes (covers almost everything we will discuss in class)
 - Various websites such as e.g.: www.play-hookey.com
 - The book “Contemporary Logic Design”, which was used in previous iterations of the class and you may have already

MULTIPLEXOR/DEMULTIPLEXOR


WHAT IS A MULTIPLEXOR?



2:1 MUX

 


4:1 MUX

 

EQUATIONS OF MUX

S1	S0	Q0
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

8:1 MUX

 


MUX AS DESIGN BLOCK

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


MUX AS DESIGN BLOCK

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

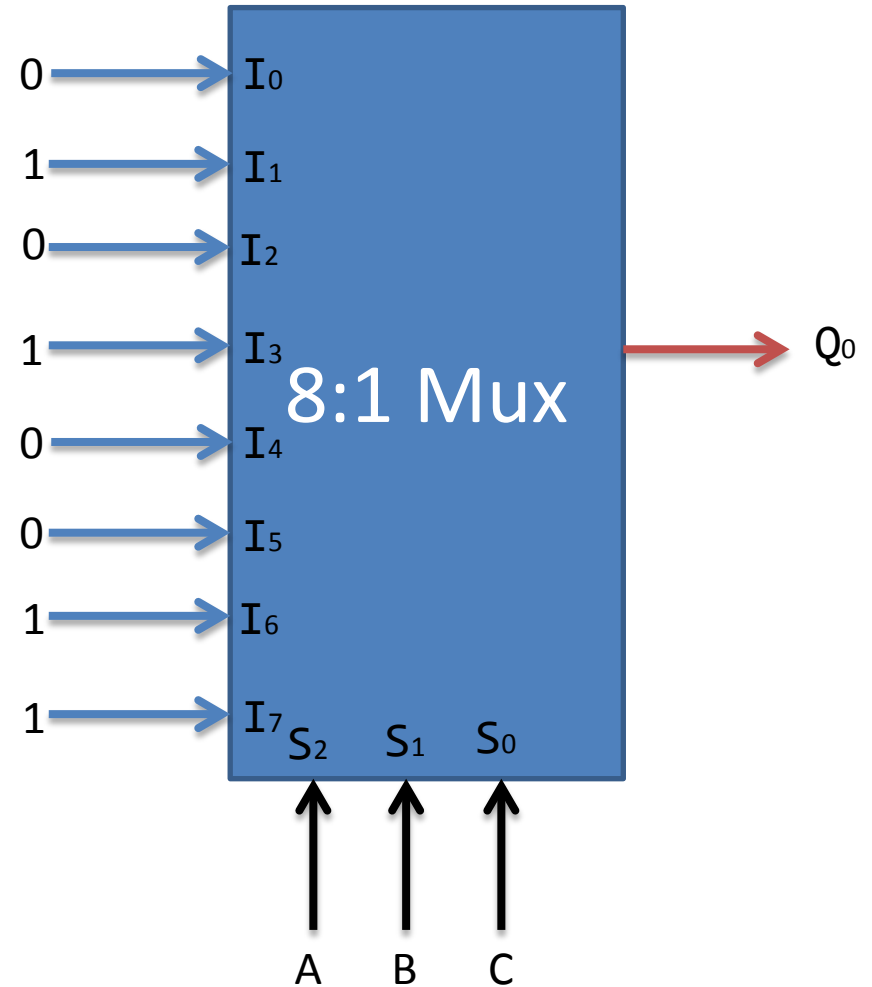

MUX AS A DESIGN BLOCK



C D		A B			
		0 0	0 1	1 1	1 0
0	0				
	1				
1	1				
	0				

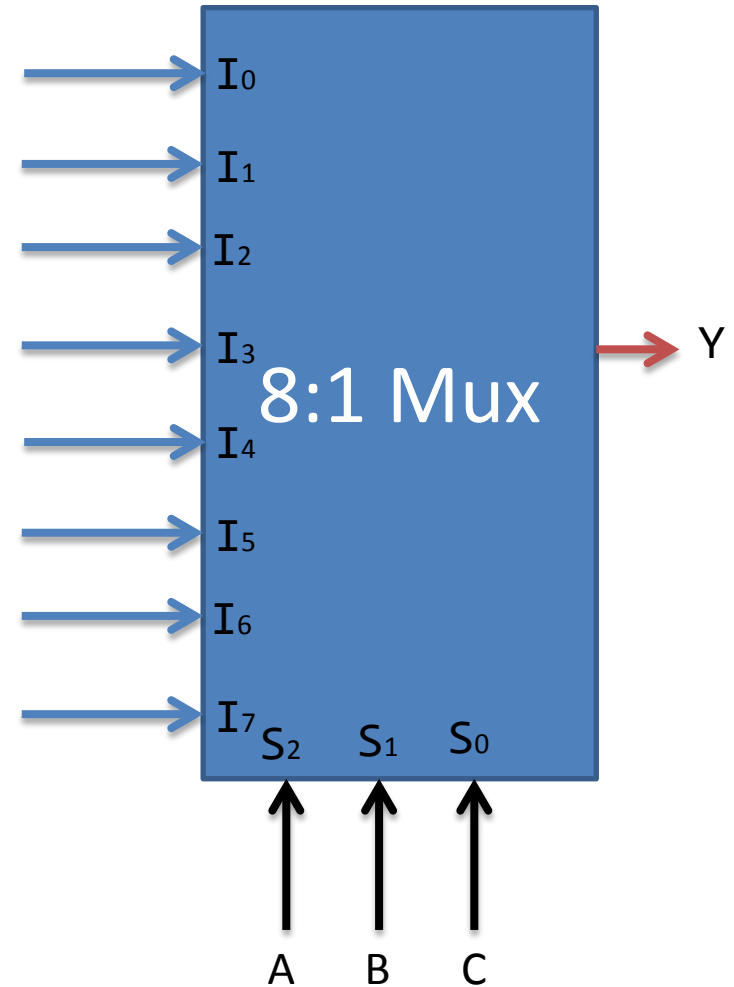

WHAT IS A DEMULTIPLEXOR?




2:4 DECODER / DEMUX

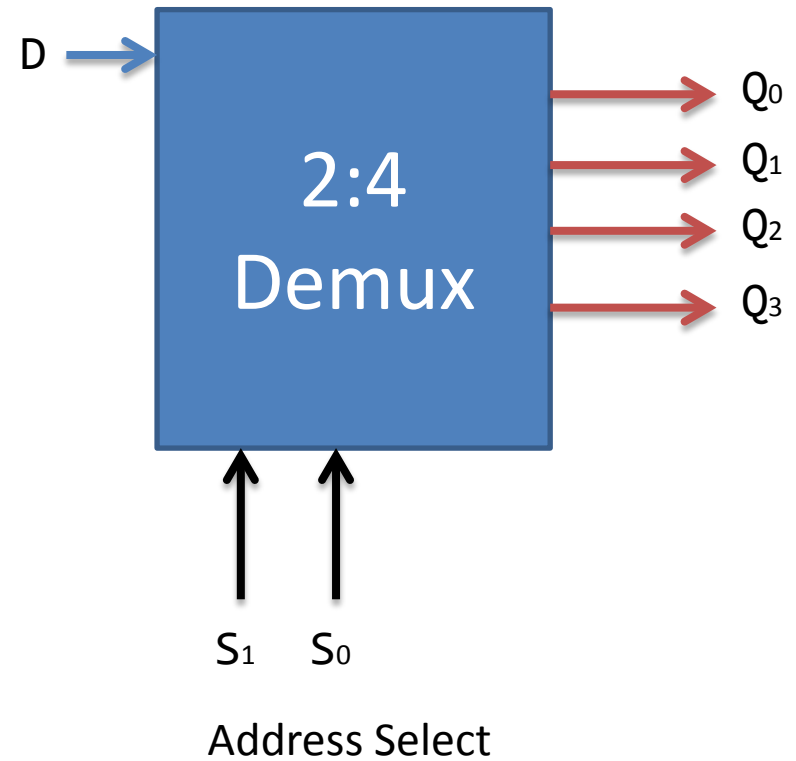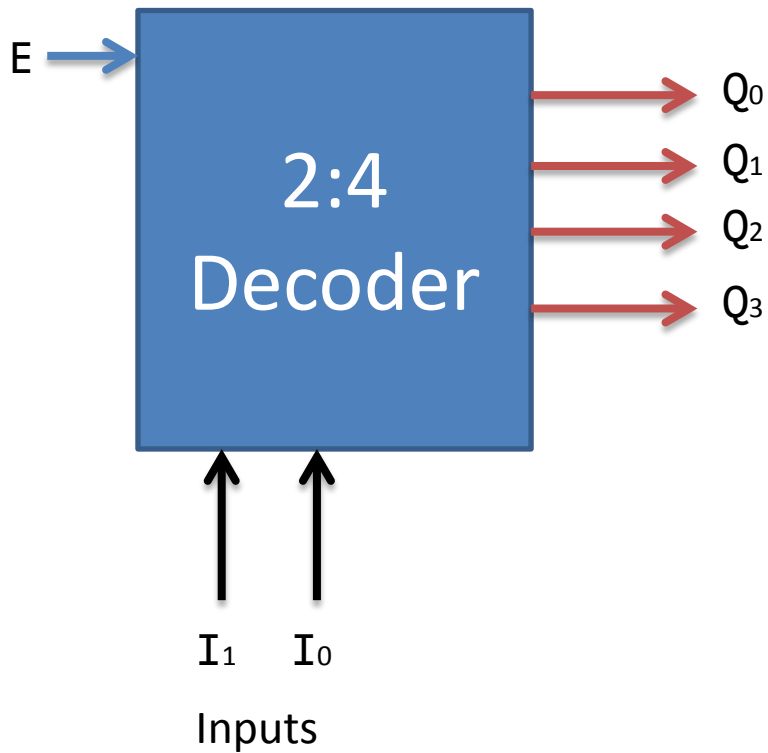


NOTATION INFORMATION

- When using ‘Enable’ (tie to ‘1’), we have a *decoder*. When inputting data, we have *demultiplexor (demux)*.
- Naming:
 - Decoder/demux named by “control signals:outputs” (e.g.: 2:4)
 - Mux named by “inputs:outputs” (e.g.: 4:1)

DECODER AS A DESIGN BLOCK

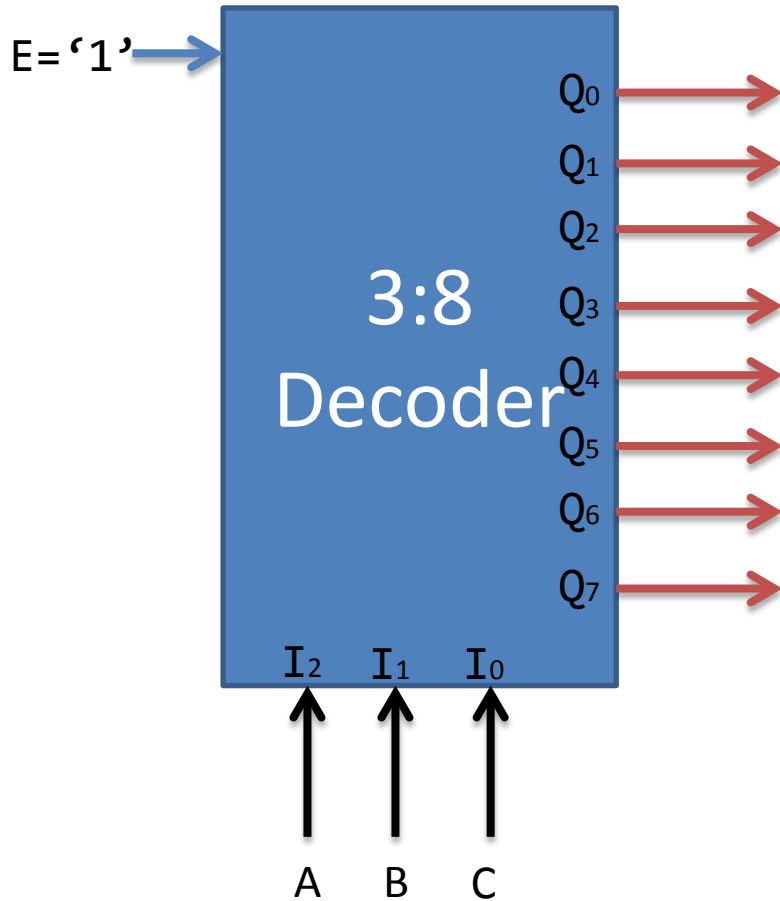


DECODER AS A MINTERM GENERATOR

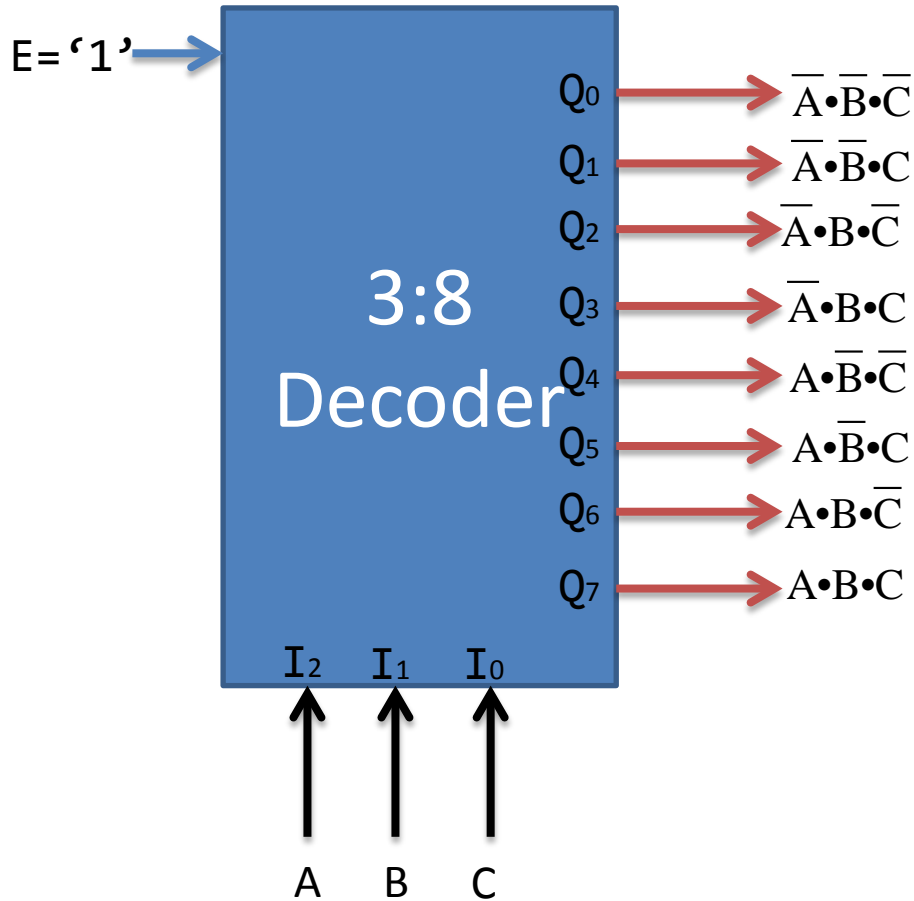


TRI-STATE GATES



INVERTER

 


3-STATE BUFFER

 

A	E	Q
0	1	0
1	1	1
0	0	Z
1	0	Z

USES FOR 3-STATE BUFFERS

 

REFERENCES

See class notes “Beyond Simple Logic Gates”
(page 133)