

ECED2200 – DIGITAL CIRCUITS



Counters

GENERAL NOTES



- See updates to these slides: www.newae.com/teaching
- These slides licensed under '[Creative Commons Attribution-ShareAlike 3.0 Unported License](http://creativecommons.org/licenses/by-sa/3.0/)'
- These slides are not the complete course – they are extended in-class
- You will find the following references useful, see www.newae.com/teaching for more information/links:
 - The book “Bebop to the Boolean Boogie” which is available to Dalhousie Students
 - Course notes (covers almost everything we will discuss in class)
 - Various websites such as e.g.: www.play-hookey.com
 - The book “Contemporary Logic Design”, which was used in previous iterations of the class and you may have already

DIVIDE-BY N COUNTER


DIVIDE-BY N

 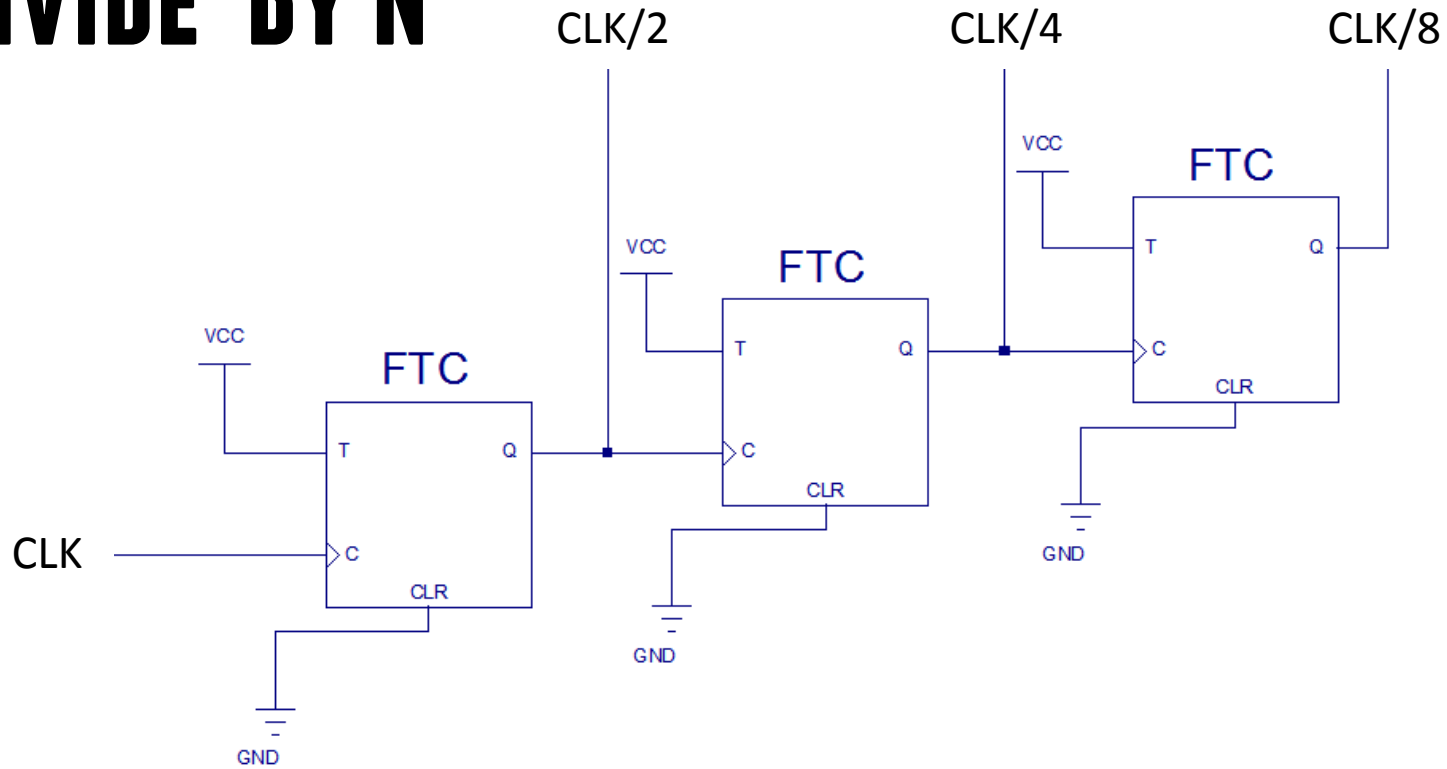

DIVIDE-BY N

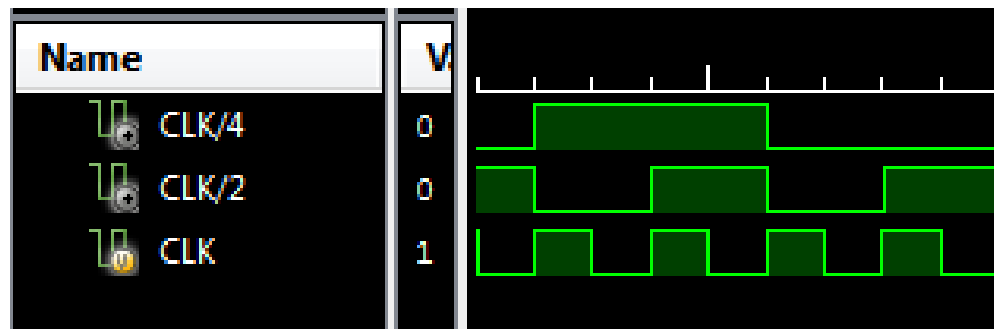 

USES OF DIVIDE-BY-N

 

USES OF DIVIDE-BY-N




32.768 KHz crystal



$$2^{15} = 32768$$

BINARY RIPPLE COUNTER



BINARY RIPPLE DESIGN

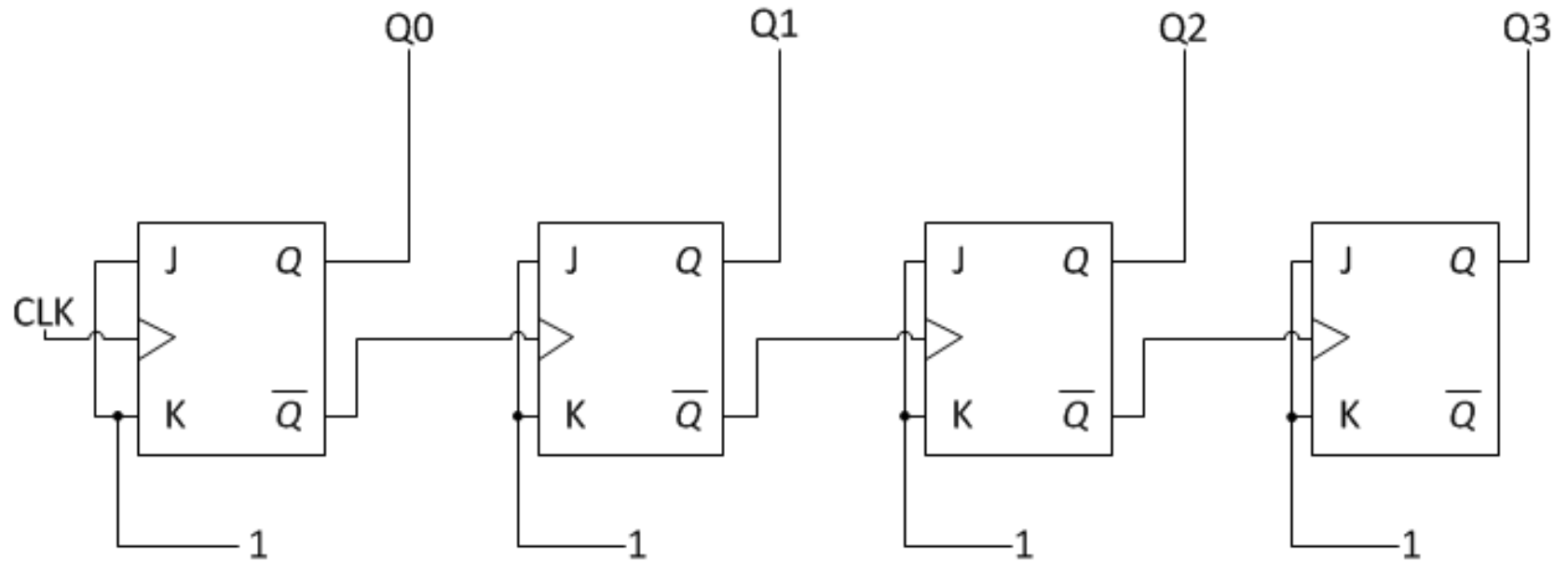


UP COUNTER

 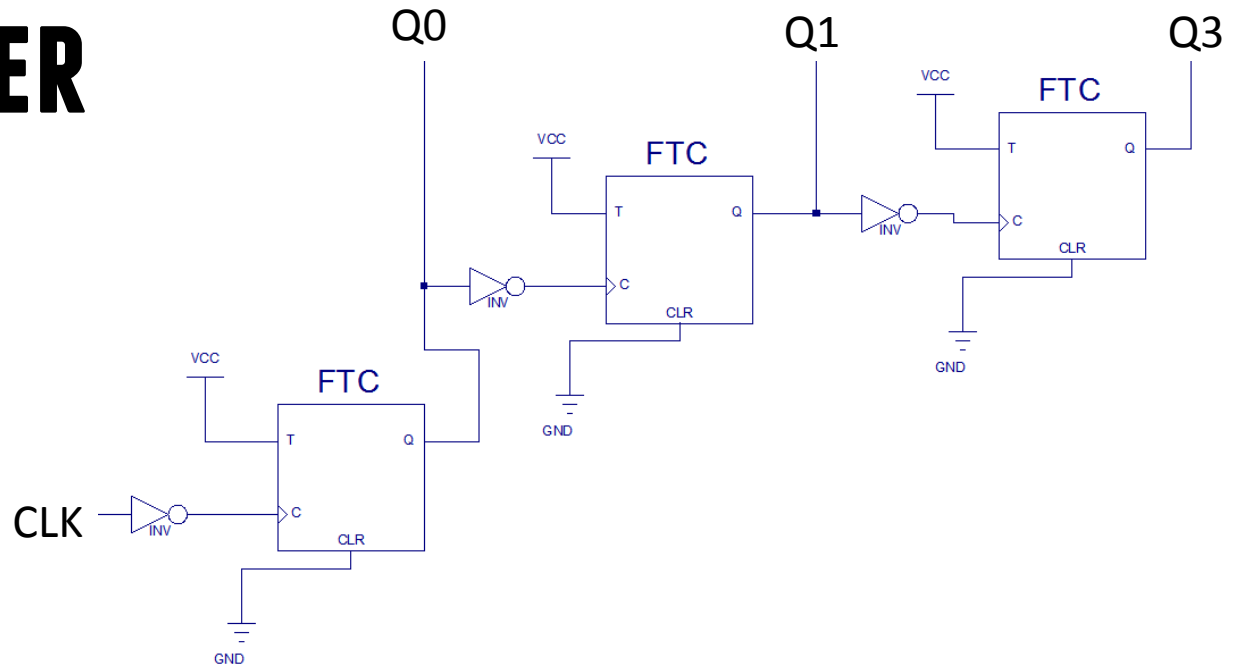

DOWN COUNTER

 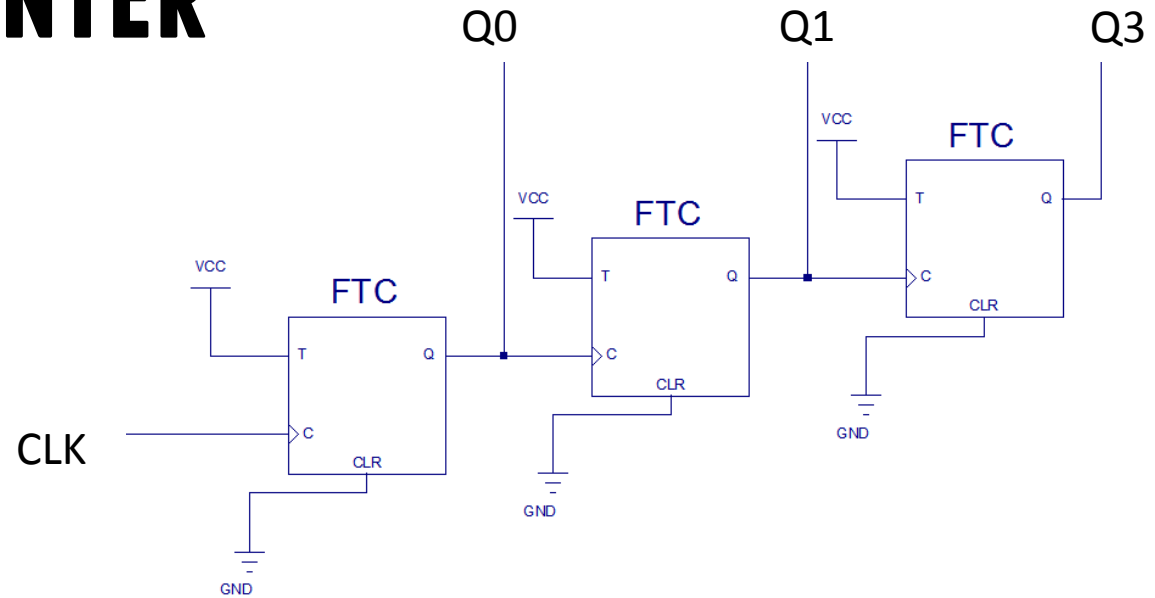


SYNCHRONOUS COUNTER

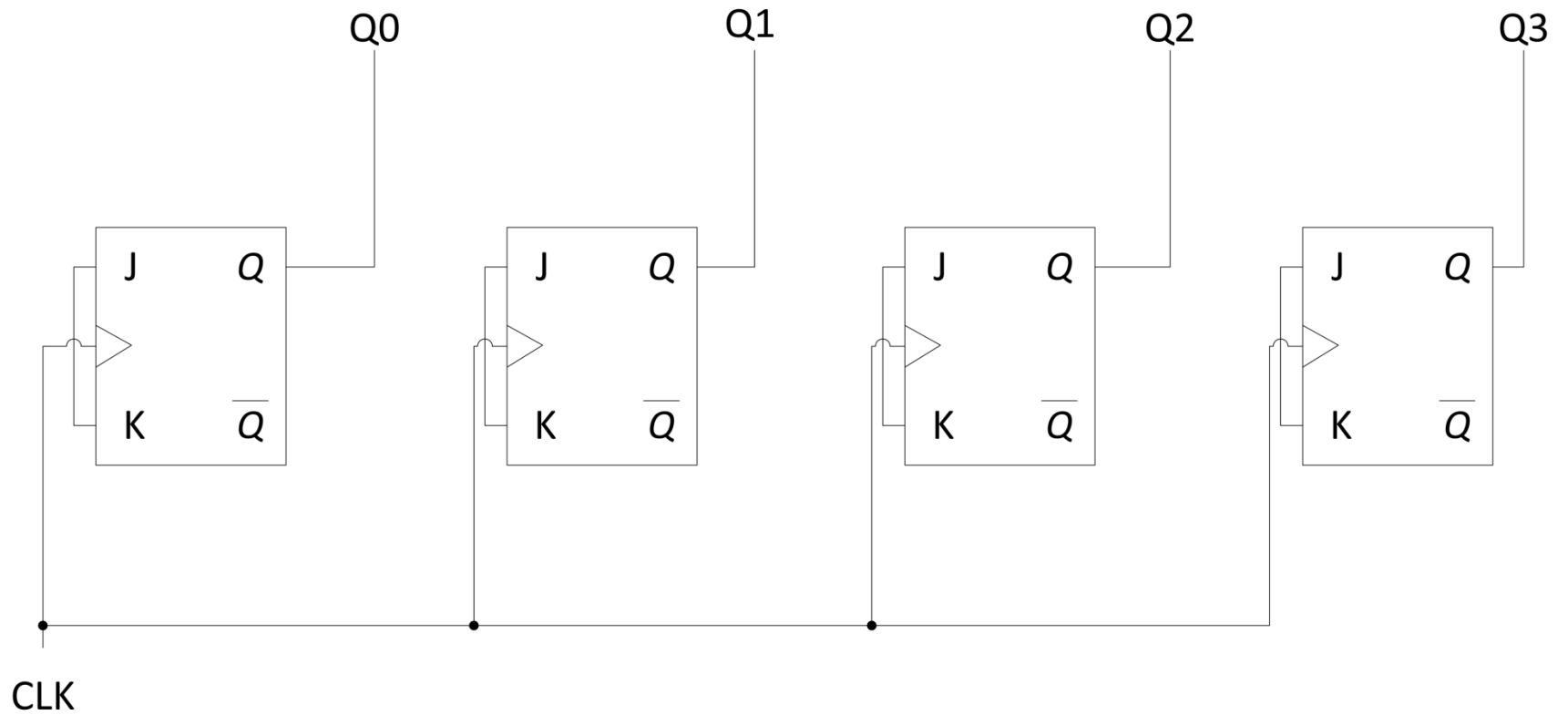


COUNT SEQUENCE?

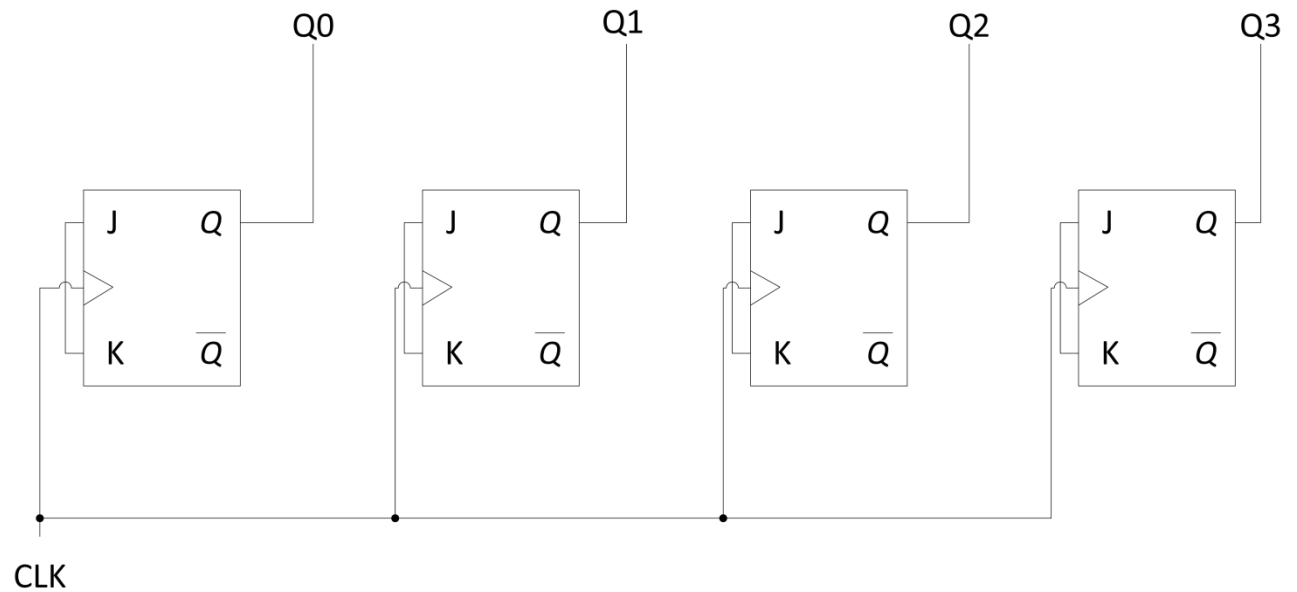0 0 0 0
0 0 0 1
0 0 1 0
0 0 1 1
0 1 0 0
0 1 0 1
0 1 1 0
0 1 1 1
1 0 0 0




SYNCHRONOUS COUNTER DESIGN

 

RING COUNTER



DESIGN

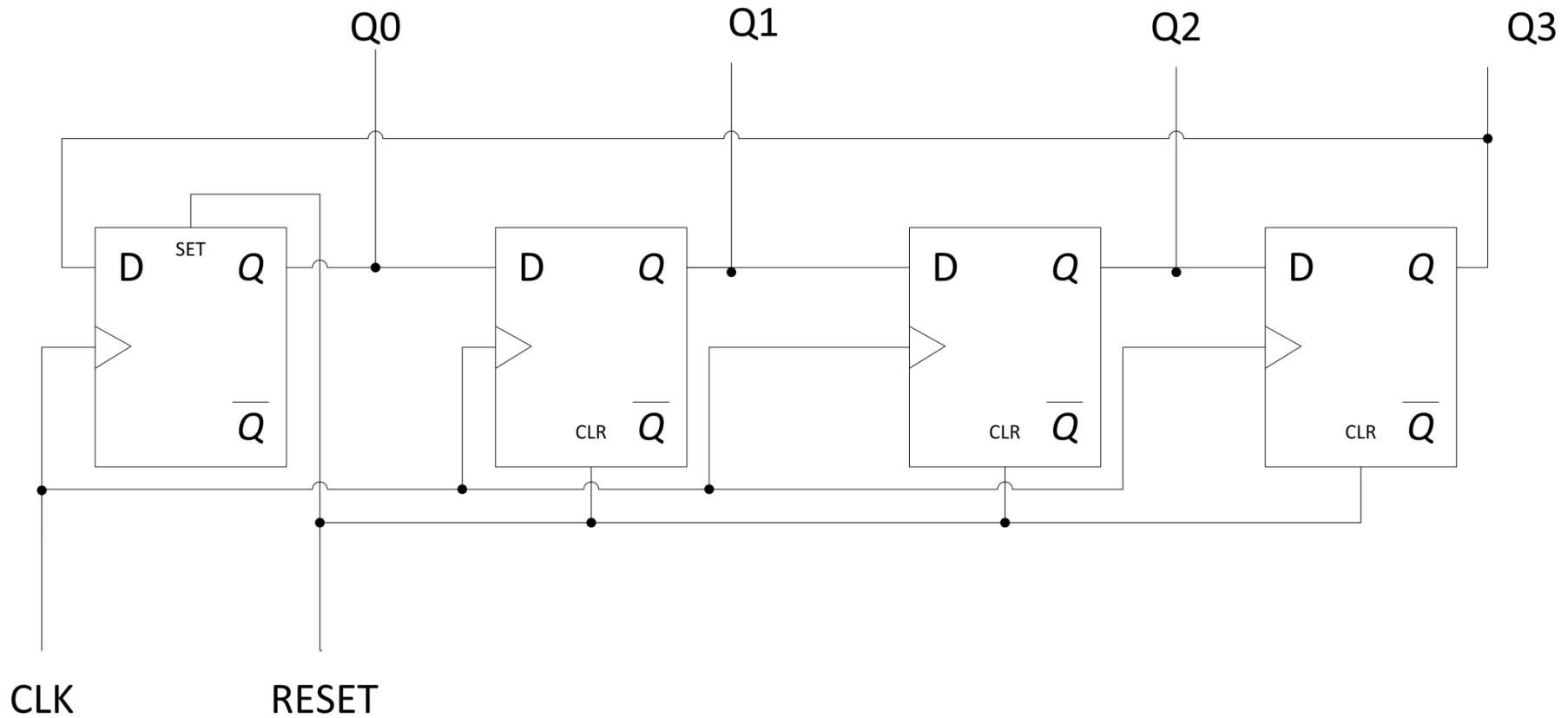

DESIGN PROCEDURE FOR ARBITRARY COUNTERS

DESIGN SPECS

0 0 0

0 1 0

0 1 1

1 0 1

1 1 0

(0, 2, 3, 5, 6)

PROCEDURE

1. Draw state transition diagram
2. Write state transition table
3. Choose flip-flops & determine required inputs
4. Design logic to realize required inputs

COUNTER DESIGN EXAMPLE

0 0 0

0 1 0


0 1 1

1 0 1

1 1 0

(0, 2, 3, 5, 6)

1. STATE TRANSITION DIAGRAM

 

2. STATE TRANSITION TABLE

A	B	C	A ⁺	B ⁺	C ⁺
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

2. STATE TRANSITION TABLE

A	B	C	A ⁺	B ⁺	C ⁺
0	0	0	0	1	0
0	0	1	?	?	?
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	?	?	?
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	?	?	?

3. SELECT FLIP-FLOP

e.g.: We will use T flip-flops:

Q	Q+	T
0	0	0
0	1	1
1	0	1
1	1	0

3. FIGURE OUT FF INPUTS

Q	Q+	T
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C	A+	B+	C+	TA	TB	TC
0	0	0	0	1	0			
0	0	1	?	?	?			
0	1	0	0	1	1			
0	1	1	1	0	1			
1	0	0	?	?	?			
1	0	1	1	1	0			
1	1	0	0	0	0			
1	1	1	?	?	?			

3. FIGURE OUT FF INPUTS

Q	Q+	T
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C	A ⁺	B ⁺	C ⁺	TA	TB	TC
0	0	0	0	1	0	0	1	0
0	0	1	?	?	?	?	?	?
0	1	0	0	1	1	0	0	1
0	1	1	1	0	1	1	1	0
1	0	0	?	?	?	?	?	?
1	0	1	1	1	0	0	1	1
1	1	0	0	0	0	1	1	0
1	1	1	?	?	?	?	?	?

4. GENERATE REQUIRED LOGIC

A	B	C	TA
0	0	0	0
0	0	1	?
0	1	0	0
0	1	1	1
1	0	0	?
1	0	1	0
1	1	0	1
1	1	1	?

		A B					
		0 0	0 1	1 1	1 0		
C	0						
	1						

4. GENERATE REQUIRED LOGIC

A	B	C	TB
0	0	0	1
0	0	1	?
0	1	0	0
0	1	1	1
1	0	0	?
1	0	1	1
1	1	0	1
1	1	1	?


		A B					
		0 0	0 1	1 1	1 0		
C	0						
	1						

4. GENERATE REQUIRED LOGIC


A	B	C	TC
0	0	0	0
0	0	1	?
0	1	0	1
0	1	1	0
1	0	0	?
1	0	1	1
1	1	0	0
1	1	1	?

		A B					
		0 0	0 1	1 1	1 0		
C	0						
	1						

4. IMPLEMENT

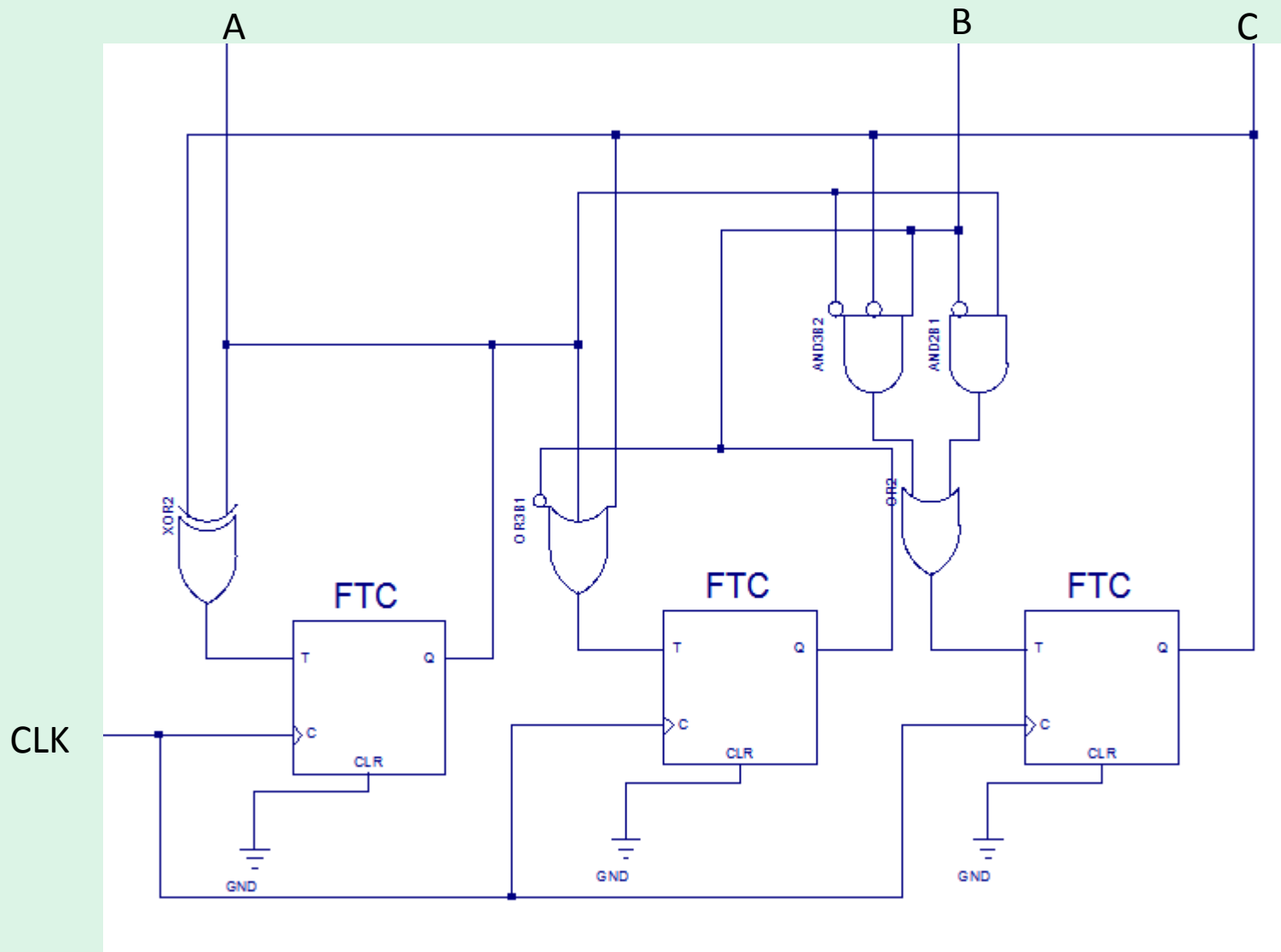


4. IMPLEMENT

 

VERIFYING IF COUNTERS ARE SELF-STARTING

A	B	C	A ⁺	B ⁺	C ⁺	TA	TB	TC
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

STATE TRANSITION DIAGRAM

 

MORE

See class notes for lots of examples of creating counters & verifying if they are self-starting or not