

```

-----
-- Example Mealy State machine. SW1 is 'ON' and SW2 is 'OFF'
-- By Colin O'Flynn 2012. Released into the public domain.
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity io_connections is
  Port (
    --Reset and Clocks
    RST      : in STD_LOGIC;
    CLK1HZ   : in STD_LOGIC;
    CLK25KHZ : in STD_LOGIC;

    --Input Switches
    SW1      : in  STD_LOGIC;
    SW2      : in  STD_LOGIC;
    SW3      : in  STD_LOGIC;
    SW4      : in  STD_LOGIC;
    SW5      : in  STD_LOGIC;

    --Output LEDs
    LED1     : out STD_LOGIC;
    LED2     : out STD_LOGIC;
    LED3     : out STD_LOGIC;
    LED4     : out STD_LOGIC;
    LED5     : out STD_LOGIC;
    LED6     : out STD_LOGIC;
    LED7     : out STD_LOGIC;
    LED8     : out STD_LOGIC
  );
end io_connections;

architecture Behavioral of io_connections is
  -- Build an enumerated type for the state machine
  type state_type is (sOn, sOff);

  -- Register to hold the current state
  signal state : state_type;

  signal sw_off : STD_LOGIC;
  signal sw_on  : STD_LOGIC;
  signal lamp   : STD_LOGIC;
  signal buzzer : STD_LOGIC;

begin
  --Give signals nicer names
  sw_on <= SW1;
  sw_off <= SW2;
  LED1 <= lamp;
  LED2 <= lamp;
  LED3 <= lamp;
  LED4 <= lamp;

  LED7 <= buzzer;

  --The following chunk of code does the state transitions.
  --It simply transitions between the ON and OFF state depending
  --if one of the inputs is held high
  process (CLK1HZ, RST)

```

```
begin
  if RST = '1' then
    state <= sOff;
  elsif (rising_edge(CLK1HZ)) then
    -- Determine the next state synchronously, based on
    -- the current state and the input
    case state is
      when sOff=>
        if sw_on = '1' then
          state <= sOn;
        else
          state <= sOff;
        end if;
      when sOn=>
        if sw_off = '1' then
          state <= sOff;
        else
          state <= sOn;
        end if;
      end case;
    end if;
  end process;

  -- Since this is a mealy state machine, we determine the
  -- outputs based on current inputs in addition to state
  -- Here we are doing this asynchronously
  process (state, sw_on, sw_off)
  begin
    case state is
      when sOn=>
        lamp <= '1';
        if sw_off = '1' then
          buzzer <= '1';
        else
          buzzer <= '0';
        end if;

        when sOff=>
          lamp <= '0';
          if sw_on = '1' then
            buzzer <= '1';
          else
            buzzer <= '0';
          end if;
        end case;
    end process;

  end Behavioral;
```